

# Rangkaian seri


1.  $R_B = 30k$

$V = 5V$

$R = ?$

$$= 30k - 10k - 15k = 5k \Omega$$

$$= 5k \Omega$$


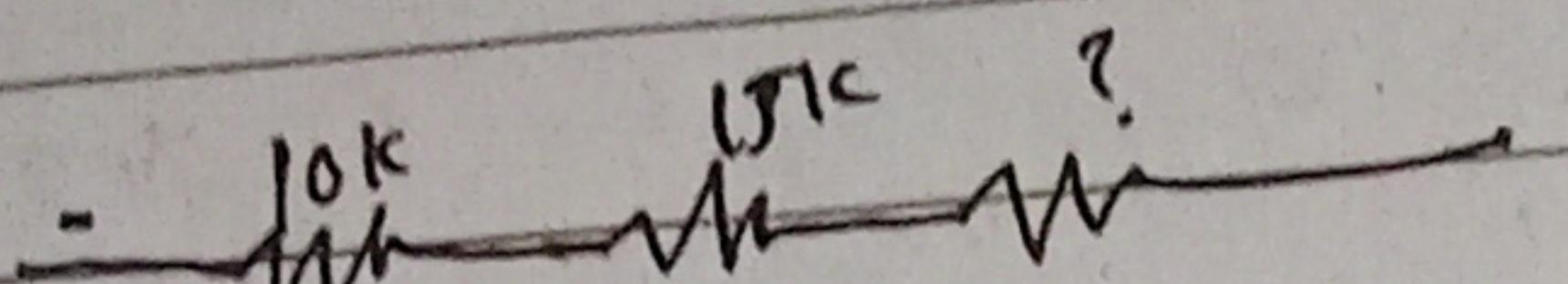


2.  $V = 15V$

$R_B = ?$

$$= 25.5k + 70 + 150 = 25.72 \Omega$$

$$R_B = 25.72 \Omega$$

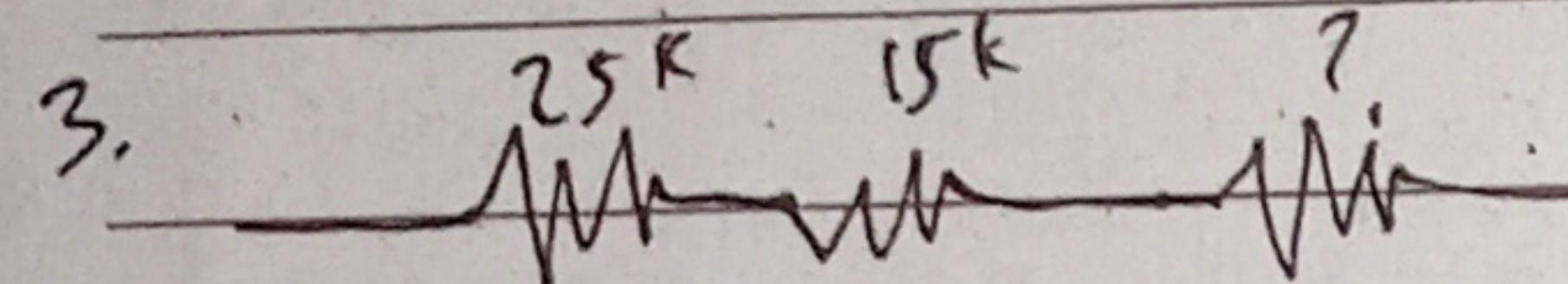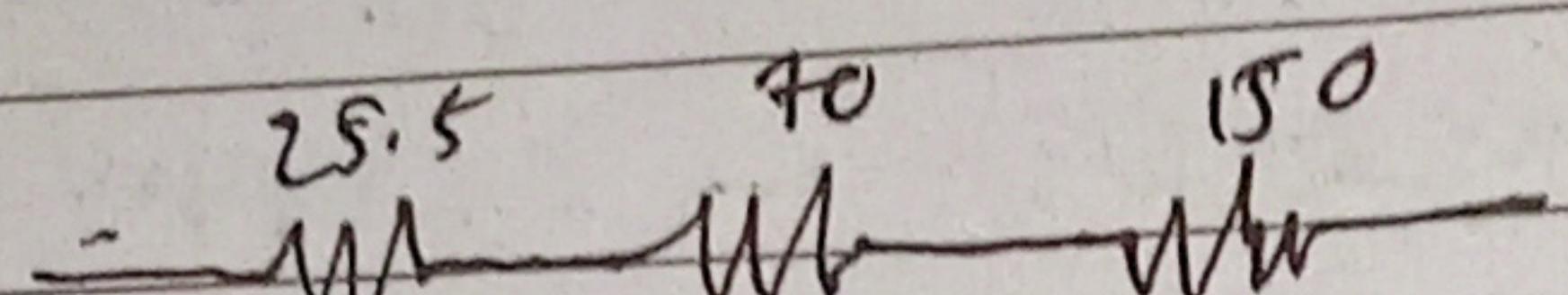

$R_B = 100k$

$V = 5V$

$R_3 = ?$

$$= 100k - 25k - 15k = 60k \Omega$$

$I = ?$

$$\frac{5}{100k} = 0.00005 A$$

## Nilai Resistor

1. Hijau Biru Hitam perak =  $53 \Omega$  10%

2. kuning Merah Merah emas =  $420 \Omega$  5%

3. Hijau Hijau Oran perak =  $55 k\Omega$  20%

4. Oran Oran kuning perak =  $330 k\Omega$  10%

5. Abu hitam Merah emas =  $810 \Omega$  5%

6. Ungu hijau hitam perak =  $75 \Omega$  20%


7. Ungu Merah Ungu perak =  $720 \Omega$  10%

8. Hijau hijau hijau emas =  $5.5 M\Omega$  20%

9. Biru hijau Oran emas =  $65 k\Omega$  5%

10. Kuning hijau hijau biru emas =  $45 M\Omega$  20%

1.

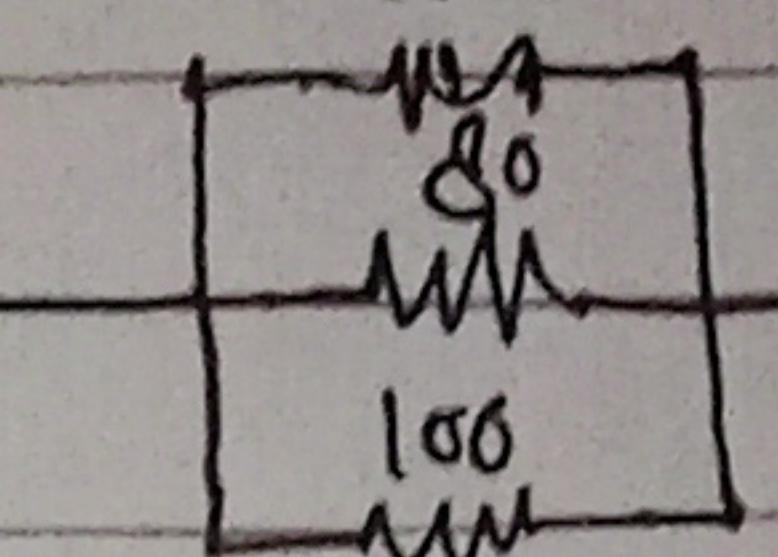


$$\frac{1}{R_E} = \frac{1}{15} + \frac{1}{15}$$

$$\frac{1}{R_E} = \frac{1}{15k} + \frac{1}{15k}$$

$$= \frac{45}{15k}$$

2.

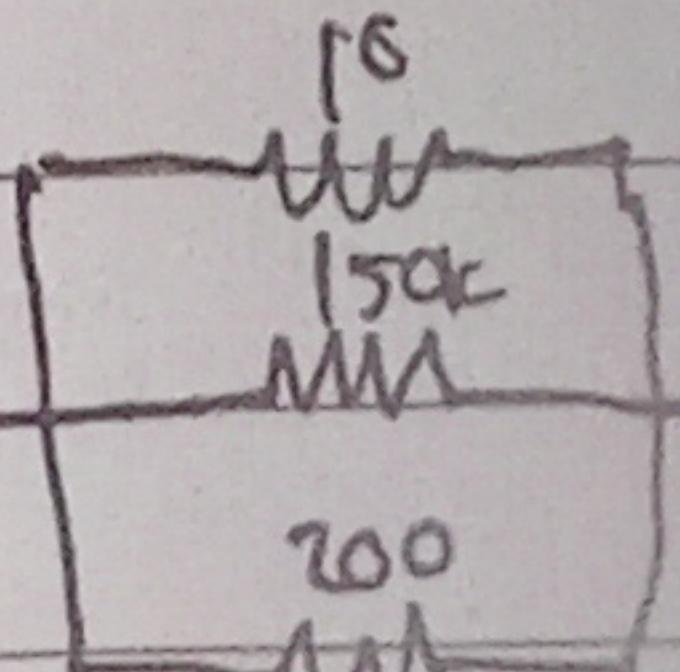

$R_E = ?$


$R_E = 1$

$R_E = 1$

No.


Date

## Resistor parallel

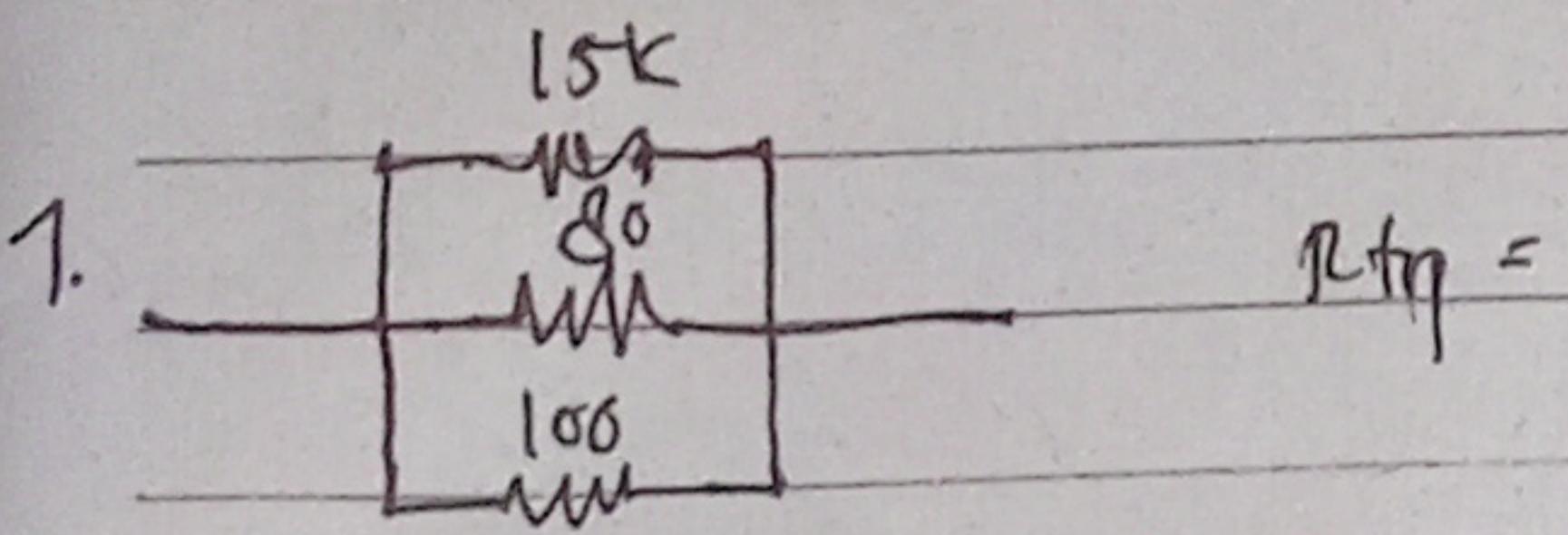

$$\frac{1}{R_E} = \frac{1}{15} + \frac{1}{50} + \frac{1}{100}$$

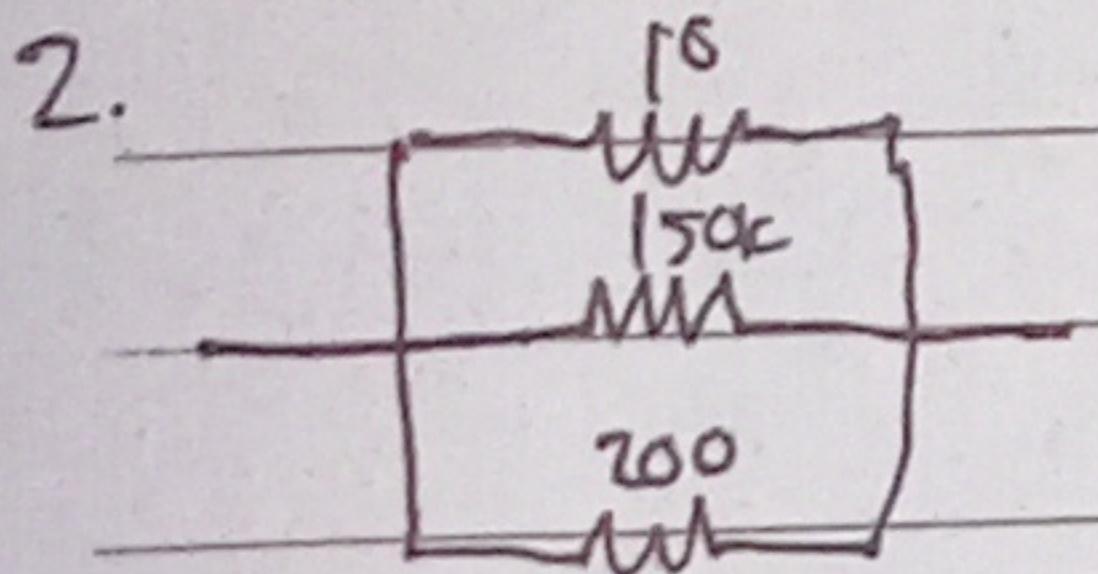
$$\begin{aligned} \frac{1}{R_E} &= \frac{1}{15k} + \frac{1}{15k} + \frac{1}{15k} \\ &= \frac{1}{15k} + 15k = 33,25 \Omega \\ \frac{1}{15k} &= 451 \end{aligned}$$



$$R_E = ?$$

$$R_E = \frac{1}{150k} + \frac{1}{150k} + \frac{1}{200}$$
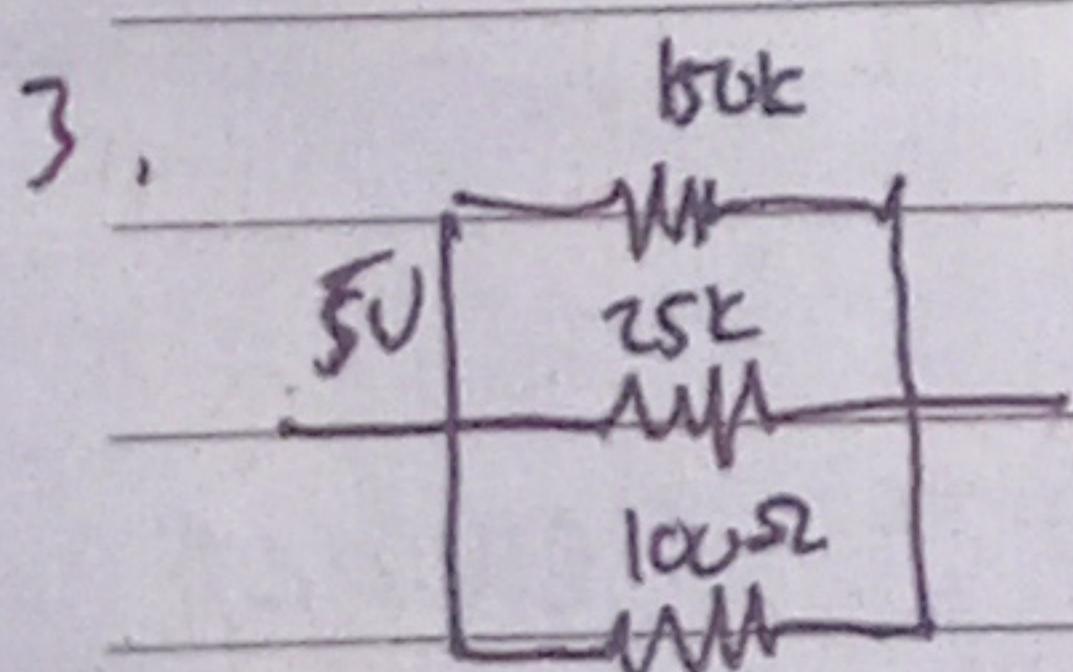
$$\begin{aligned} R_E &= \frac{1}{150k} + \frac{15k}{150k} + \frac{750}{150k} \\ &= \frac{1}{150k} + \frac{150k}{150k} = 9,52 \Omega \end{aligned}$$




$$I_1 = ? = I = \frac{5}{150k} = 0,0003 A$$

$$I_2 = ? = I = \frac{5}{25k} = 0,0002 A$$

$$I_3 = ? = I = \frac{5}{100} = 0,05 A$$

No. \_\_\_\_\_

Date \_\_\_\_\_

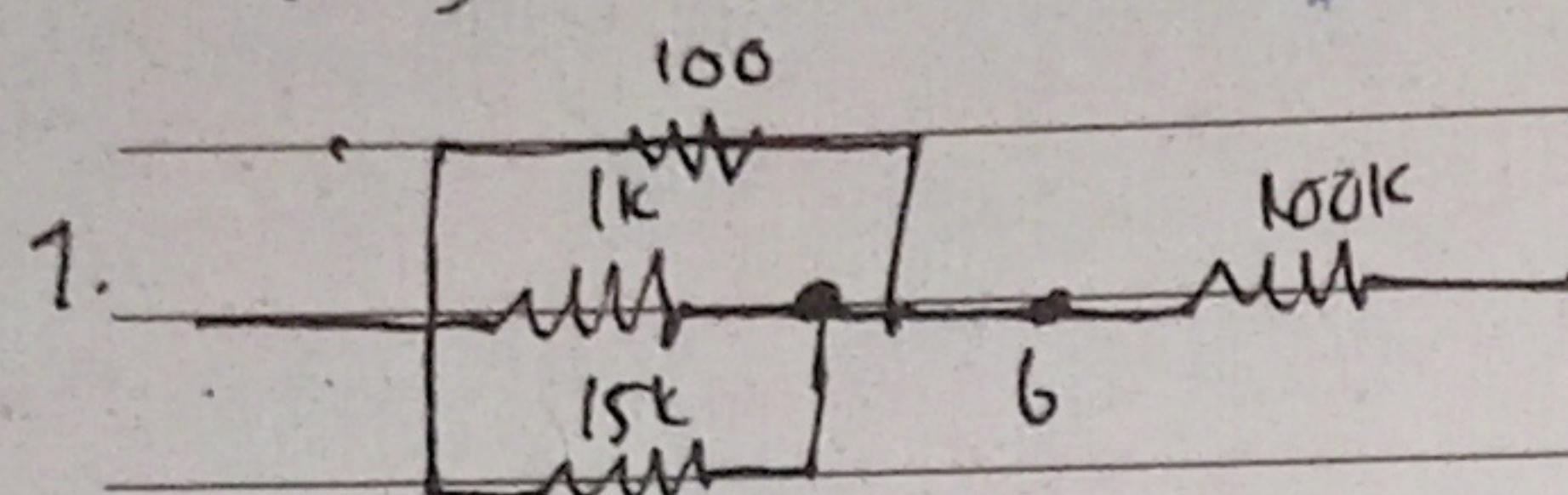Rangkaian kombinasi

$$R_t = ?$$

$$R_{tp} = \frac{1}{R_t} = \frac{1}{100} + \frac{1}{100} + \frac{1}{15000} = \frac{1}{10} + \frac{1}{10} + \frac{15}{1000} = \frac{1000}{26} = \frac{1000}{26} = 38.4$$

$$R_t = 38.4$$


$$R_t = 38.4 + 100k = 100,038 \Omega$$

2. berapa  $V_{bc}$  bila  $I = 2A$ 

$$V = I \cdot R$$

$$= 2 \cdot 100,038 \Omega$$

$$= 200,076 V = 2 KV$$

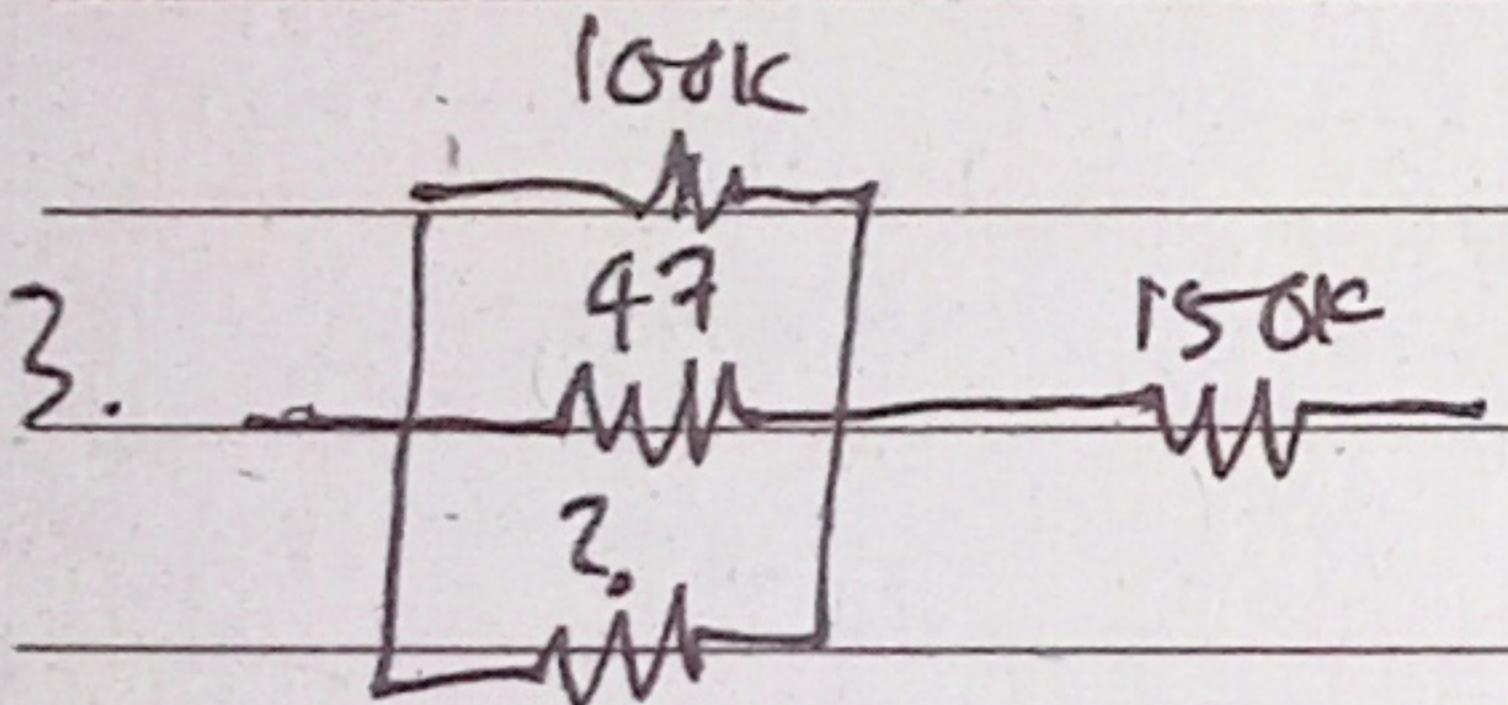

$$\text{bila } I = 2A$$

$$V = 15 V$$

$$R_3 = ?$$

1.  $R = \frac{V}{I} = \frac{15}{2} = 7,5 \Omega$

2.  $I = \frac{18.000.147}{1000}$

3.  $\frac{I}{R_k} = \frac{I}{100k} + \frac{I}{47k} + \frac{I}{R_3}$

4.  $\frac{I}{R_k} = \frac{1000}{18.000.147} = 0.000055 \quad 150 k \times 0.000055 = 7,5 \Omega$

5.  $\frac{I}{R_k} = \frac{100 + 47 + 18m}{100}$